

Nirma University

Institute of Technology

Semester End Examination (IR/RPR), May - 2024

Bachelor of Science (Computer Science and Engineering), Semester-I

B. Tech. in CL / CH / ME / EE / CSE, Semester-II

B. Tech. in EC / EI / CSE, Semester-I

Int. B. Tech. (CSE) - MBA, Semester-II

1EE801 Electrical Science

Roll /
Exam No.

Supervisor's initial
with date

Time: 3 Hours

Max. Marks: 100

Instructions:

1. Attempt all questions.
2. Use section-wise separate answer book.
3. Figures to right indicate full marks.
4. Draw neat sketches wherever necessary.
5. Assume suitable additional data, if required.
6. All symbols and notations have their usual meaning.

SECTION - A

Q.1 (A)
CO1 BL5

Determine the equivalent resistance and the current drawn from 20 V source in the network shown in Fig. 1. [6]

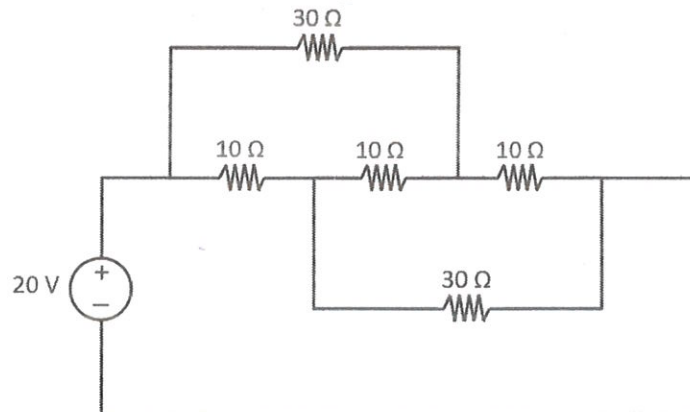


Fig. 1

Q.1 (B)
CO1 BL5

Determine the values of V_1 and V_2 in the circuit shown in Fig. 2 using nodal analysis. [6]

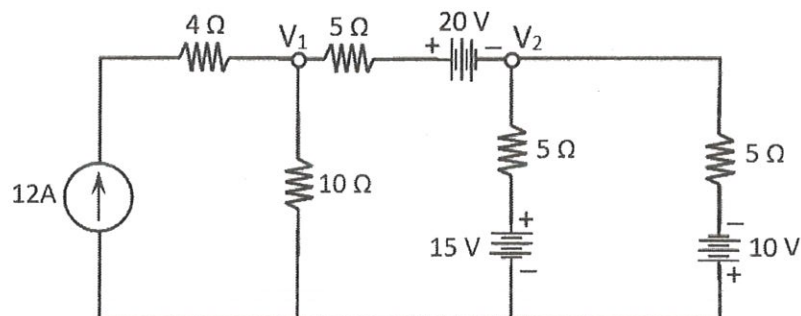


Fig. 2

- Q.1 (C)** Determine the equivalent capacitance for the circuit shown in Fig. 3 [4]
CO1 BL5 between the terminal pair A and B.

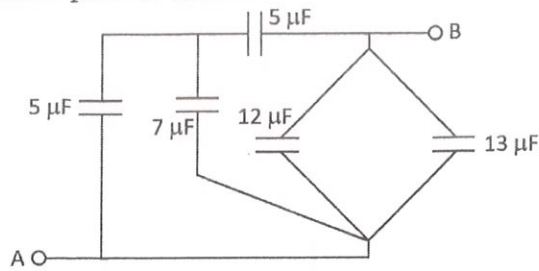


Fig. 3

- Q.2 (A)** Find the current through 20 Ω resistor in the network shown in Fig. 4 [6]
CO1 BL5

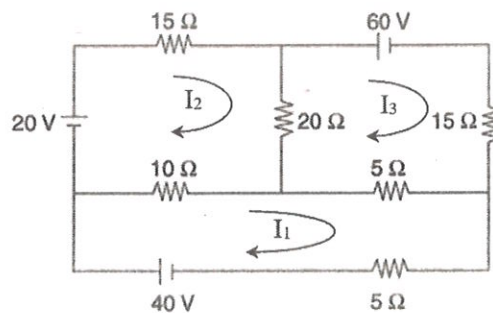


Fig. 4

- Q.2 (B)** Determine the current through 20 ohm resistor using superposition theorem for the network shown in Fig. 5. [6]
CO1 BL5

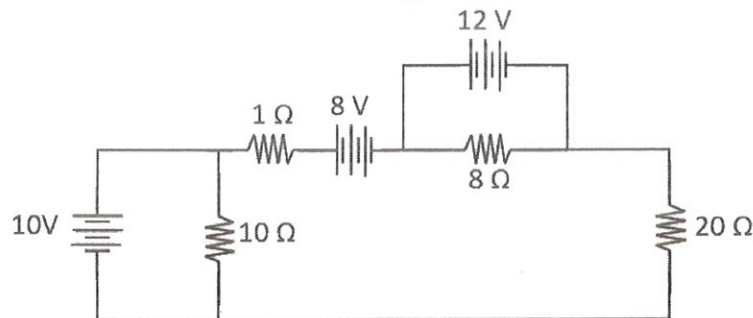


Fig. 5

- Q.2 (C)** Define time constant of a RC circuit. Evaluate the charging voltage and charging current during the charging of a capacitor at 1τ , 2τ , 3τ , 4τ and 5τ . Plot voltage and current variations. [4]
CO1 BL3
- Q.3 (A)** What are the factors that govern the reluctance of a magnetic circuit? Illustrate with neat sketch the concept of series and parallel magnetic circuits. [6]
CO2 BL2
- Q.3 (B)** A series RC circuit consumes a power of 7000 W when connected to 250 V, 50 Hz supply. The voltage across the resistor is 130 V. Calculate (i) resistance (ii) current (iii) power factor (iv) capacitance (v) impedance (vi) write the equations for $v(t)$ and $i(t)$. [6]
CO2 BL5
- Q.3 (C)** In a RLC series circuit, $R = 5 \Omega$, $L = 2 \text{ mH}$, and $C = 1 \mu\text{F}$. Determine (i) resonant frequency (ii) voltage across resistor (iii) voltage across inductor (iv) voltage across capacitor (v) quality factor (vi) comment on the results obtained. [6]
CO2 BL5

SECTION - B

- Q.4 (A)** Two circuits with impedances of $Z_1 = (20 + j20) \Omega$ and $Z_2 = (10 - j10) \Omega$ are connected in parallel. If the supply current is 10 A, Determine: (i) the power dissipated in each branch (ii) assuming the supply current of 10 A at reference, determine the source voltage in its rectangular and polar form. [6]
CO2 BL5
- Q.4 (B)** When the three identical star-connected coils are supplied with 440V, 50 Hz, 3-phase supply, the 1-phase wattmeter whose current coil is connected in line R and pressure coil across the phase R and neutral reads 6 kW and the ammeter connected in R-phase reads 30 Amp. Assuming RYB phase sequence. find: [6]
CO2 BL5
- the power factor of the circuit
 - resistance of the coil
 - reactance of the coil
 - reactive power of 3-phase load
 - apparent power of 3-phase load
 - Comment on the results obtained
- Q.4 (C)** The input power to a three-phase motor was measured by two wattmeter method. The readings were 10.4 kW and -3.4 kW and the voltage was 400 V. Calculate the power factor and the line current. [4]
CO2 BL5
- Q.5 (A)** A 40-0-40 V (rms) centre tapped transformer is used with a full wave rectifier circuit having an internal resistance of diode $r_d = 1 \Omega$. If the load resistance is 19Ω , evaluate: (i) Transformer secondary peak voltage (ii) DC output current (iii) DC output power (iv) AC input power (v) rectifier efficiency (vi) voltage across each diode. [6]
CO3 BL5
- Q.5 (B)** Explain, how a bipolar junction transistor works as an amplifier? [4]
CO3 BL2
- Q.5 (C)** Enumerate various special purpose diodes. Explain the construction, operating principle and applications of any one type of diode. [6]
CO3 BL2
- Q.6 (A)** Design the simplest possible logic circuit that implements the output of the logic circuit shown in Fig. 6 with necessary equations and truth table. [6]
CO4 BL6

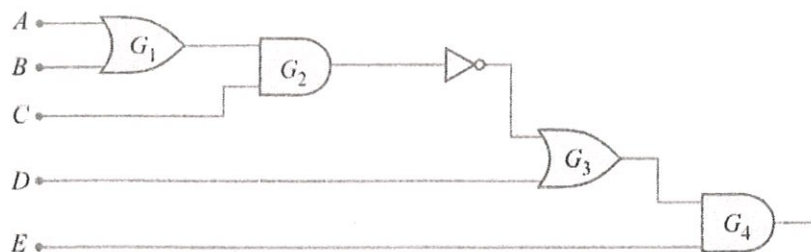


Fig. 6

- Q.6 (B)** Show that any logic circuit can be designed using a NOR gate and NAND gate. [6]
CO4 BL3
- Q.6 (C)** Convert the following: [6]
CO4 BL3
- $(B2F)_{16}$ to octal,
 - $(24.6)_8$ to decimal and
 - $(76)_{10}$ to octal number.

Nirma University
Institute of Technology
 Supplementary Examination (SPE), August - 2023
 B. Tech. in CL / CH / ME / EE, Semester-II
 Int. B. Tech. (CSE) - MBA, Semester-II
 1EE801 Electrical Science

Roll /
Exam No.

Supervisor's initial
with date

Time: 3 Hours

Max. Marks: 100

Instructions:

1. Attempt all questions.
2. Use section-wise separate answer book.
3. Figures to right indicate full marks.
4. Draw neat sketches wherever necessary.
5. Assume suitable additional data if required.
6. All symbols and notations have their usual meaning.

SECTION - A

- Q.1 (A)** Make use of mesh analysis to find the current through $4\ \Omega$ resistor in the network shown in Fig. 1. [6]
 CO1 BL3

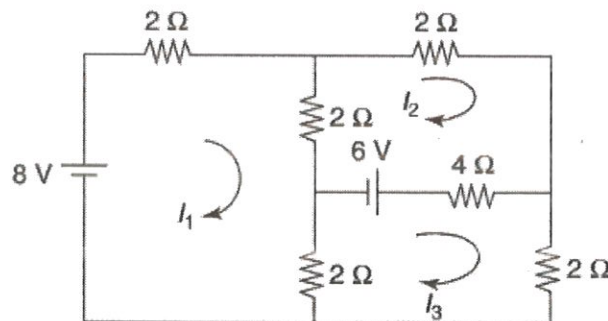


Fig. 1

- (B)** Calculate the current through the $5\ \Omega$ resistor for the network shown in Fig. 2 using nodal analysis. [6]
 CO1 BL3

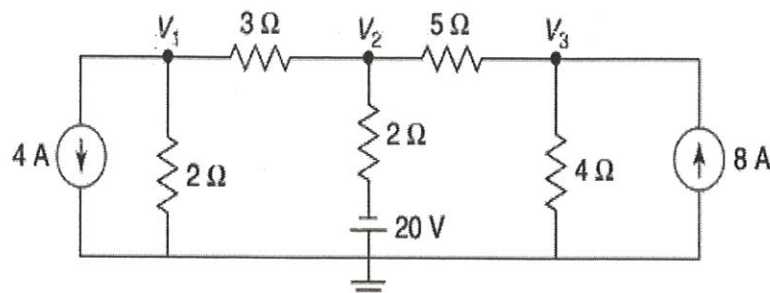


Fig. 2

- (C)** Explain Superposition theorem and discuss the steps involved to solve the circuit. [4]
 CO1 BL2

Q.2 (A) Discuss electrolytic capacitor. Also, derive the expression for energy stored in capacitor. [4]
CO1 BL2

(B) Use star delta transformation to determine the equivalent resistance between terminal pair A-B of the network shown in Fig. 3. [6]
CO1 BL3

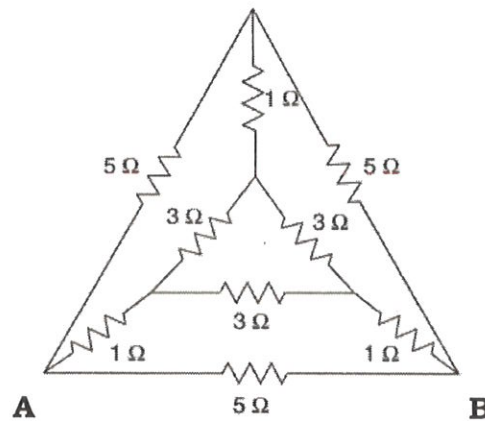


Fig. 3

(C) Use Thevenin's theorem to evaluate the current through $2\ \Omega$ resistor of the network shown in Fig. 4. [6]
CO1 BL3

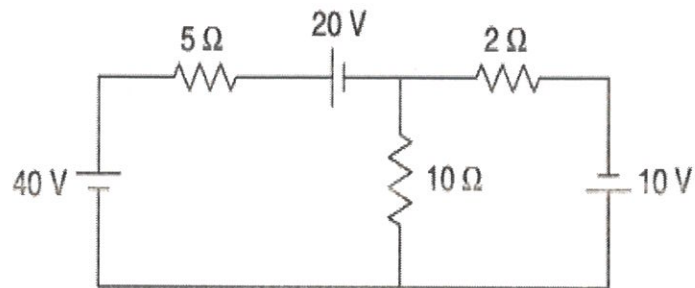


Fig. 4

Q.3 (A) What do you mean by active power, reactive power and apparent power? Also, derive the relationship between them. [6]
CO2 BL2

(B) A coil having resistance of $10\ \Omega$ and inductance of $21\ \text{H}$ is connected across a d.c. voltage of $150\ \text{V}$. Calculate: (a) the value of current at $0.5\ \text{sec.}$ after switching on the supply, (b) during the decay of current the time it would take to reach a value of $8\ \text{A}$ from its maximum value after switching off the supply [6]
CO2 BL5

(C) A load of $22\ \text{kW}$ operates at 0.8 lagging power factor when connected to a $240\ \text{V}$, single-phase, $50\ \text{Hz}$ source. Determine (a) current in the load, (b) power factor angle, (c) impedance, (d) resistance of load, (e) reactance of load, (f) voltage and current equations. [6]
CO2 BL4

Section B

- Q.4 (A)** What are the advantages of three phase system over single-phase system? [4]
CO2 BL2
- (B)** A three-phase 500 V motor load has a power factor of 0.4 lagging. [4]
CO2 BL5 Two wattmeters connected to measure the power show the input to be 30 kW. Calculate the reading on each wattmeter.
- (C)** A symmetrical three phase, 400 volts system supplies a balanced [6]
CO2 BL5 delta connected load. The current in each delta branch is 30 A and its phase angle is 37° lagging with respect to voltage across each branch. Find the line current and total power. Draw the phasor diagram showing all currents and voltages.
- Q.5 (A)** A crystal diode having internal resistance $r_f = 20 \Omega$ is used for half [6]
CO3 BL5 wave rectification. If the applied voltage $v = 60 \sin \omega t$ and the load resistance $R_L = 800 \Omega$. Evaluate (i) maximum current (ii) DC current (iii) AC power input (iv) DC power output (v) DC output voltage (vi) efficiency of rectification.
- (B)** Write short notes on special purpose diodes. [6]
CO3 BL2
- (C)** Explain the working of NPN transistor as a switch and an amplifier. [6]
CO3 BL2
- Q.6 (A)** Why NAND gate is called as universal gate? Demonstrate the [6]
CO4 BL3 following three gates with the help of NAND gates:
i) AND gate
ii) OR gate
iii) NOT gate
- (B)** Simplify the following Boolean expression to a minimum number of [6]
CO4 BL4 literals and draw the logic circuit and write their truth tables.
$$Y = \bar{A}\bar{B}C + A\bar{B}C + AB\bar{C} + ABC \quad ; \quad Y = A\bar{B}D + A\bar{B}\bar{D}$$
- (C)** Develop the logic circuit diagram and truth table of a full adder using [6]
CO4 BL4 two half adders.

Nirma University

Institute of Technology

Supplementary Examination (SPE), February - 2024

B. Tech. in CH / EC / CSE / EI Engineering, Semester-I

Bachelor of Science (Computer Science and Engineering), Semester-I

1EE801 Electrical Science

Roll /
Exam No.

Supervisor's initial
with date

Time: 3 Hours

Max. Marks: 100

Instructions:

1. Attempt all questions.
2. Use section-wise separate answer book.
3. Figures to right indicate full marks.
4. Draw neat sketches wherever necessary.
5. Assume suitable additional data if required.
6. All symbols and notations have their usual meaning.

SECTION - A

- Q.1 (A)** Apply suitable method to determine the current I through $2\ \Omega$ resistor in the circuit shown in Fig.1. [6]
CO1 BL5

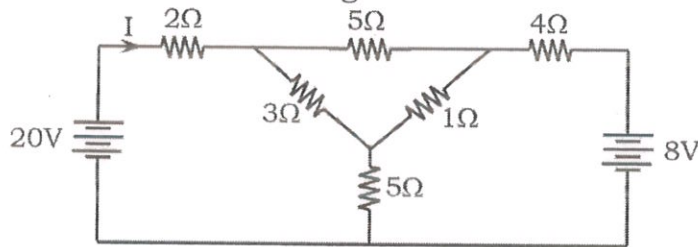


Fig. 1

- Q.1 (B)** Apply nodal method to determine the current through $4\ \Omega$ resistor in the circuit shown in Fig.2. [6]
CO1 BL5

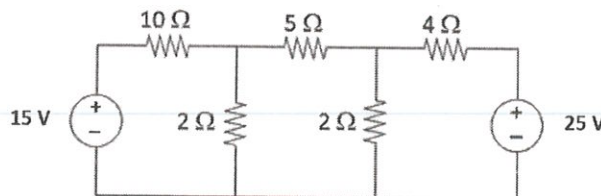


Fig. 2

- Q.1 (C)** Deduce an expression for charging voltage of a capacitor in series RC circuit when supplied by a DC source voltage. [4]
CO1 BL5
- Q.2 (A)** State and explain Thevenin's theorem using illustrative example. [6]
CO1 BL2

- Q.2 (B)** Determine the power dissipation in $4\ \Omega$ resistor of the circuit shown in Fig. 3 using mesh analysis. [6]
CO1 BL5

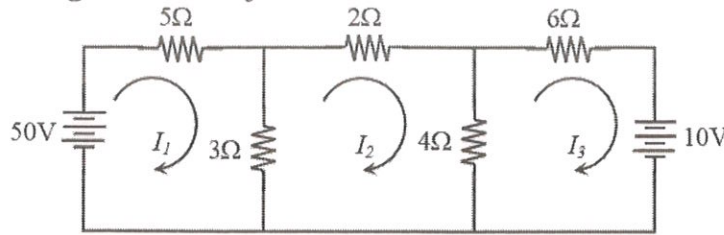


Fig.3

- Q.2 (C)** Two capacitors have capacitances of $6\ \mu\text{F}$ and $10\ \mu\text{F}$ respectively. Find the total capacitance when they are connected in (a) parallel and in (b) series. When the above two capacitances are connected in series across a $200\ \text{V}$ supply, find the potential difference across each capacitor and the charge on each capacitor. [4]
CO1 BL5
- Q.3 (A)** Deduce the equation for decay of current in R-L series circuit. Discuss the role of time constant. [6]
CO2 BL5
- Q.3 (B)** Define the following terms with respect to magnetic circuit. [6]
CO2 BL2
- Magneto-motive force
 - Magnetic field strength
 - Reluctance
 - Permeability
 - Mean length of magnetic path
 - Leakage flux
- Q.3 (C)** A resistance of $40\ \Omega$ and an inductor of $70\ \text{mH}$ are connected in parallel across a $200\ \text{V}$, $50\ \text{Hz}$ supply. Evaluate: (i) current drawn from the supply (ii) apparent power and (iii) reactive power (iv) impedance (v) power factor (vi) phase angle between voltage and current [6]
CO2 BL5

SECTION - B

- Q.4 (A)** A star connected load has an impedance of $(3 + j4)\ \Omega$ in each phase and is connected across a balanced three phase delta connected alternator having line voltage of $200\ \text{volts}$. Calculate the (i) line current (ii) phase voltage across the alternator (iii) phase voltage across the load (iv) impedance per phase (v) average power (vi) phase angle. [6]
CO2 BL5
- Q.4 (B)** Evaluate the RMS value, average value and form factor of the waveform shown in Fig. 4. [6]
CO2 BL5

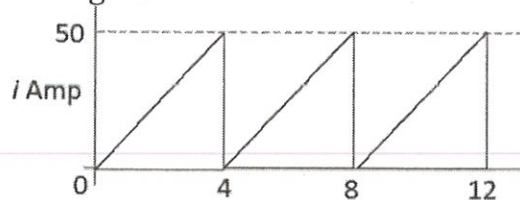


Fig. 4

- Q.4 (C)** Discuss few merits of three phase systems. [4]
CO2 BL2
- Q.5 (A)** Appraise the phenomenon of transistor as an amplifier using [6]
CO3 BL2
suitable example.
- Q.5 (B)** An AC supply of 230 V is applied to a half-wave rectifier circuit [6]
CO3 BL5
through a transformer of turns ratio 20:1. If the load resistance is 1000 Ω and internal resistance of diode used for half-wave rectification is 10 Ω . Determine: (i) dc output voltage (ii) ac power input (iii) dc output power (iv) dc output current (v) rectification efficiency (vi) comment on the results obtained.
- Q.5 (C)** Design a full adder circuit and discuss its operation in detail. [4]
CO3 BL5
- Q.6 (A)** i) Determine the octal value of the binary number 10010111. [6]
CO4 BL3
ii) Add 54_{10} with 28_{10} using binary numbers.
iii) Determine the MSB and the LSB of 80_{10} when expressed as an Octal number.
- Q.6 (B)** Describe the EX-OR gate. Specify its symbol and write its truth table. [6]
CO4 BL2
Develop a two input EX-OR gate using only NAND gates.
- Q.6 (C)** Design the simplest possible logic diagram that implements the [6]
CO4 BL6
output of the logic diagram shown in Fig. 5 with necessary equations and truth table.

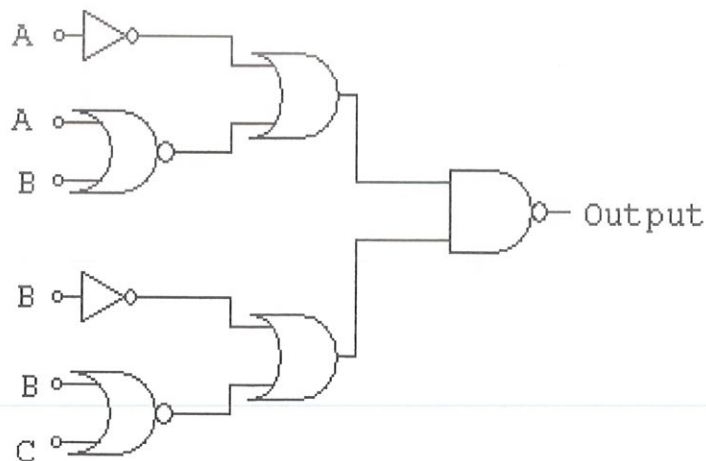


Fig. 5

Nirma University

Institute of Technology

Supplementary Examination (SPE), July - 2024

B. Tech. in CL / ME / EE / CSE, Semester-II

Int. B. Tech. (CSE) - MBA, Semester-II

1EE801 Electrical Science

Roll /
Exam No.

Supervisor's initial
with date

Time: 3 Hours

Max. Marks: 100

Instructions:

1. Attempt all questions.
2. Use section-wise separate answer book.
3. Figures to right indicate full marks.
4. Draw neat sketches wherever necessary.
5. Assume suitable additional data, if required.
6. All symbols and notations have their usual meaning.

SECTION - A

- Q.1 (A)** Determine the value of all resistances in the network shown in Fig. 1, if power dissipation in R_2 and R_4 are 75 W and 30 W respectively. [6]
CO1 BL5

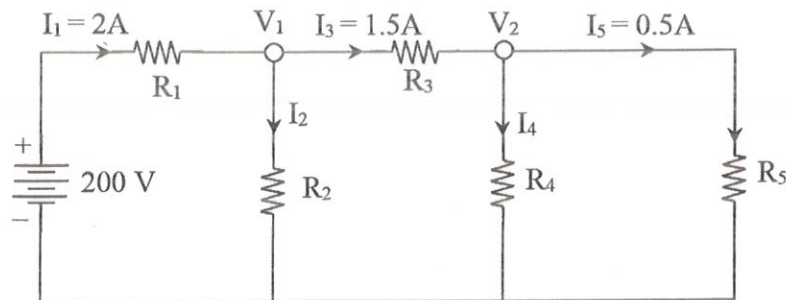


Fig. 1

- Q.1 (B)** Apply mesh analysis to determine the current through 4 Ω resistor in the circuit shown in Fig. 2. [6]
CO1 BL5

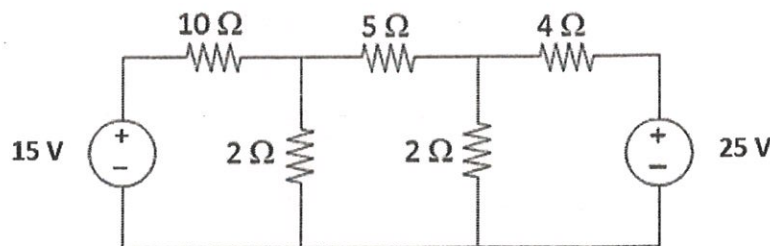


Fig. 2

- Q.1 (C)** In a RC series circuit excited by a DC voltage source, determine the percentage value of capacitor discharging current, capacitor discharging voltage and voltage across resistor at 1τ , 2τ , 3τ , 4τ and 5τ . Plot all these parameters. (τ - time constant). [4]
CO1 BL5

- Q.2 (A)** Apply star-delta transformation to find the equivalent resistance between the terminal pair A-B for the circuit shown in Fig. 3. [6]
CO1 BL3

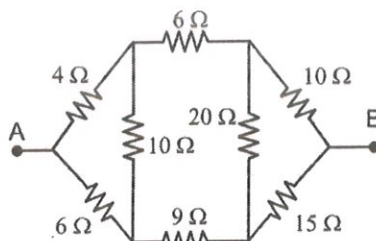


Fig. 3

- Q.2 (B)** Determine Norton's equivalent circuit across the terminal pair a-b for the circuit shown in Fig. 4. Find the current through the load resistance, if $R_L = 4\Omega$. [6]
CO1 BL5

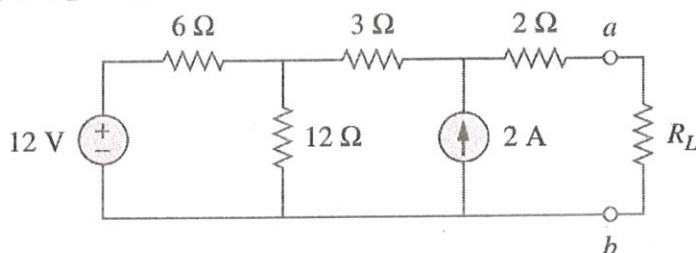


Fig. 4

- Q.2 (C)** Two capacitors A and B are connected in series across a 100 V supply and it is observed that the potential difference across them are 60 V and 40 V respectively. A capacitor of $2\mu\text{F}$ capacitance is now connected in parallel with A and the potential difference across B rises to 90 volts. Estimate the capacitance of A and B in microfarads. [4]
CO1 BL5
- Q.3 (A)** Explain with a neat sketch the concept of magnetic circuit. Tabulate the analogous parameters of magnetic circuit with the parameters of electric circuit. [6]
CO2 BL2
- Q.3 (B)** If the voltage $v(t) = V_m \sin \omega t$ is applied to a single-phase series RC circuit, prove that the current drawn is expressed as: $i(t) = I_m \sin(\omega t + \phi)$. Draw the voltage, current and power waveforms. [6]
CO2 BL5
- Q.3 (C)** In a RLC series circuit, $R = 2\Omega$, $L = 1\text{ mH}$, and $C = 0.4\mu\text{F}$. Determine (i) resonant frequency (ii) voltage across resistor (iii) voltage across inductor (iv) voltage across capacitor (v) quality factor (vi) comment on the results obtained. [6]
CO2 BL5

SECTION - B

- Q.4 (A)** Two circuits with impedances of $Z_1 = (10 + j15)\Omega$ and $Z_2 = (6 - j8)\Omega$ are connected in parallel. If the supply current is 20 A, Determine: (i) the power dissipated in each branch (ii) assuming the supply current of 20 A at reference, determine the source voltage in its rectangular and polar form. [6]
CO2 BL5

Q.4 (B) Three equal resistances connected in star across a three phase balanced supply consume 2000 watts. If the same three resistors were reconnected in delta across the same supply, determine the power consumed. Comment on the results obtained. [6]
CO2 BL5

Q.4 (C) Explain the concept of phase sequence in voltages induced in a three phase generator. [4]
CO2 BL2

Q.5 (A) Determine the currents I_1 , I_2 and I_3 for the network shown in Fig. 5. Assume silicon diodes and use simplified model. [6]
CO3 BL5

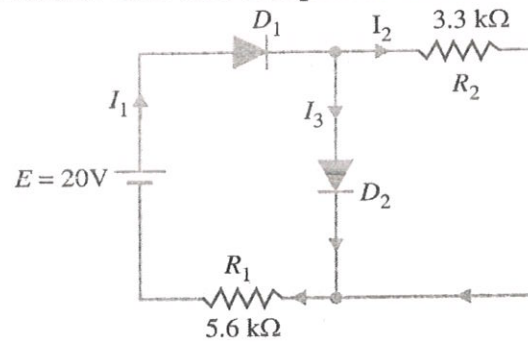


Fig. 5

Q.5 (B) Describe the construction and operating principle of a bipolar junction transistor. [6]
CO3 BL2

Q.5 (C) Enumerate various special purpose diodes. Explain the construction, operating principle and applications of any one type of diode. [4]
CO3 BL2

Q.6 (A) Design the simplest possible logic circuit that implements the output of the logic circuit shown in Fig. 6 with necessary equations and truth table. [6]
CO4 BL6

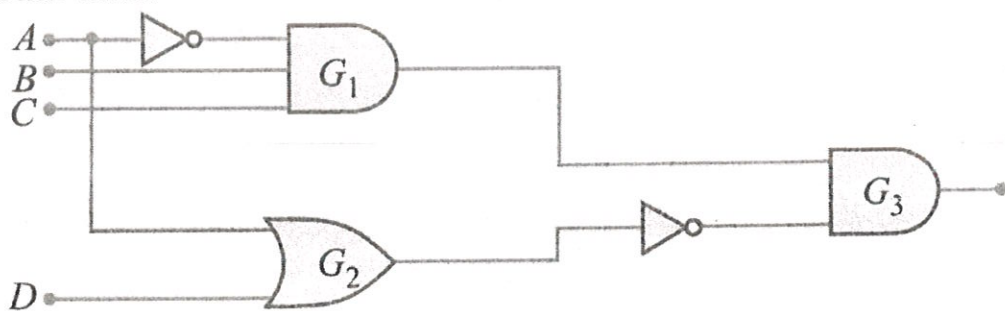


Fig. 6

Q.6 (B) Prove that when the AND product of two variables is inverted, this is equal to inverting each variable individually and then ORing them. [6]
CO4 BL5

Q.6 (C) i) Convert the following octal numbers into its binary equivalent. [6]
CO4 BL3
(76)₈, (255)₈, (372)₈

ii) What is the role of encoder and decoder in digital circuits?

Nirma University

Institute of Technology

Supplementary Examination (SPE), March - 2024

B. Tech. in Electronics and Instrumentation Engineering, Semester-I
1EE801 Electrical Science

Roll /
Exam No.

Supervisor's initial
with date

Time: 3 Hours

Max. Marks: 100

Instructions:

1. Attempt all questions.
2. Use section-wise separate answer book.
3. Figures to right indicate full marks.
4. Draw neat sketches wherever necessary.
5. Assume suitable additional data if required.
6. All symbols and notations have their usual meaning.

SECTION - A

- Q.1 (A)** Apply star delta transformation to find the equivalent resistance [6]
CO1 BL3 between the terminal pair a-b of the circuit as shown in Fig. 1.

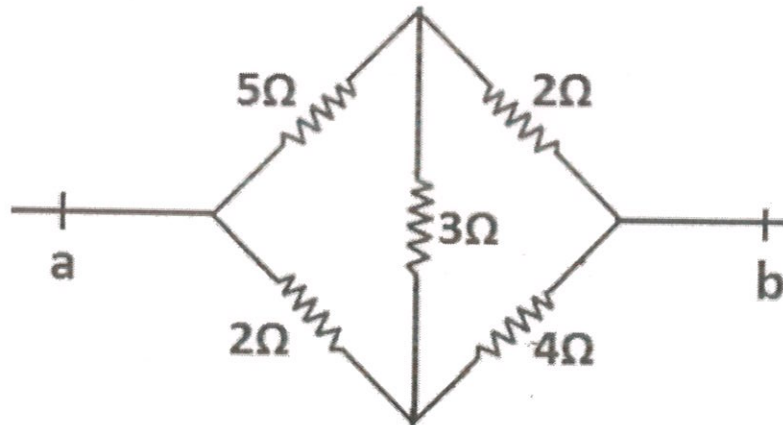


Fig. 1

- Q.1 (B)** Determine the current delivered by the source of 5 volts in the [6]
CO1 BL5 network shown in Fig. 2.

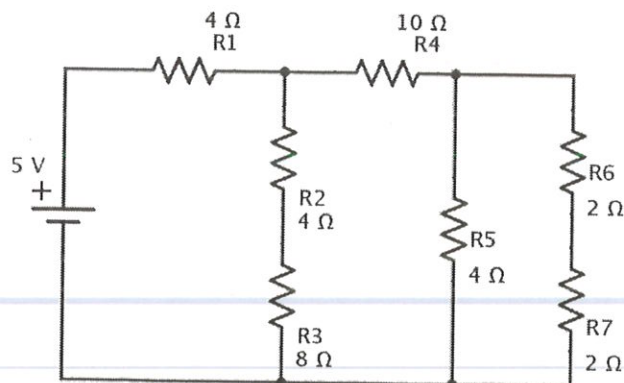


Fig. 2

Q.1 (C) Deduce the expression for current through a capacitor at any instant during the charging in an RC series circuit excited by a DC source. [4]
CO1 BL5

Q.2 (A) Explain the phenomenon of generation of alternating voltage. [4]
CO2 BL2

Q.2 (B) Apply Thevenin's theorem to find the current through $4\ \Omega$ resistor for the circuit shown in Fig. 3. [6]
CO1 BL3

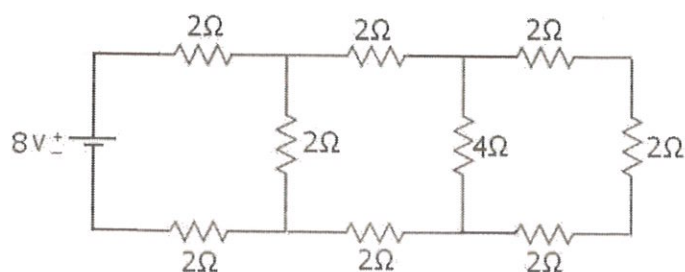


Fig. 3

Q.2 (C) Use mesh analysis to find the current through $10\ \Omega$ resistor in the network shown in Fig. 4. [6]
CO1 BL3


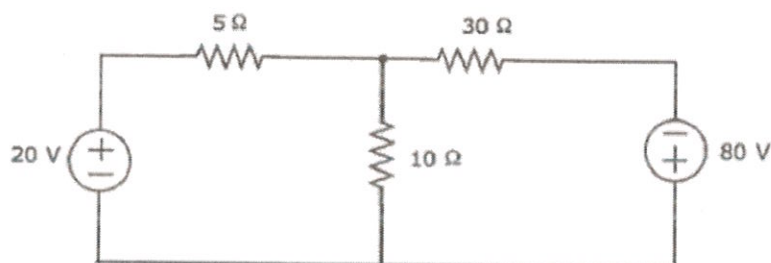


Fig. 4

Q.3 (A) Explain with neat sketch the leakage flux and fringing in a magnetic circuit. [6]
CO2 BL2

Q.3 (B) Derive an expression for two series connected coupled coils when the fluxes assist each other. [6]
CO2 BL5

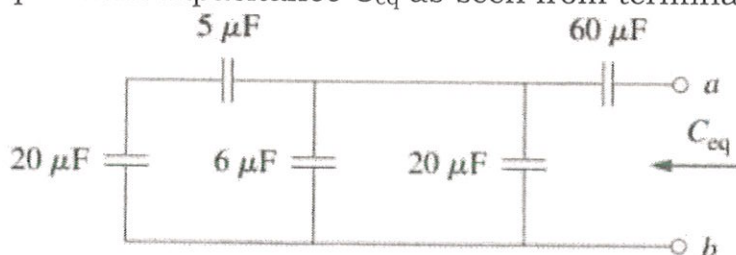Q.3 (C) Find the equivalent capacitance C_{eq} as seen from terminal pair a-b. [6]
CO1 BL5



SECTION – B

- Q.4 (A)** List few merits of three phase system over single-phase system. [4]
CO2 BL2
- Q.4 (B)** Define the following terms with reference to alternating current: [4]
CO2 BL2
i) instantaneous value ii) maximum value iii) average value iv) time period.
- Q.4 (C)** A 3-phase load consists of three star connected similar resistances, [6]
CO2 BL5
each of resistance of $100\ \Omega$. The supply is 400 V, 50 Hz. Calculate (i) line current (ii) total power consumed.
If the frequency of input voltage is changed from 50 Hz to 60 Hz, what is its effect on the line current and the total power consumed.
- Q.5 (A)** Elucidate the working of a PN junction diode. Draw and explain its [6]
CO3 BL2
forward and reverse characteristics.
- Q.5 (B)** Explain the working of a biased positive clipper and biased negative [6]
CO3 BL2
clipper.
- Q.5 (C)** Illustrate with neat sketch the working of half wave bridge rectifier [6]
CO3 BL2
circuit and draw its input and output waveforms.
- Q.6 (A)** Describe the following number systems used in digital electronics. [6]
CO4 BL2
i) Decimal number system
ii) Binary number system
iii) Octal number system
- Q.6 (B)** Give reasons, why digital circuits are preferred over analog circuits? [6]
CO4 BL2
- Q.6 (C)** Solve the following Boolean expressions: [6]
CO4 BL3
i) $Y = A + \bar{A} \cdot B$
ii) $Y = A \cdot B + A \cdot \bar{B} + B \cdot C$
iii) $Y = A \cdot B + A \cdot B \cdot C + A \cdot B \cdot \bar{C}$

Nirma University

Institute of Technology

Semester End Examination (IR/RPR), April - 2025

B. Tech. in All Programmes, Semester - I / II

Int. B. Tech. (CSE) - MBA, Semester - I / II

Bachelor of Science (CSE), Semester - I

1EE801CC22 / 1EE801 Electrical Science

Roll /
Exam No.

Supervisor's initial
with date

Time: 3 Hours

Max. Marks: 100

Instructions:

1. Attempt all questions.
2. Use section-wise separate answer book.
3. Figures to right indicate full marks.
4. Draw neat sketches wherever necessary.
5. Assume suitable additional data, if required.
6. All symbols and notations have their usual meaning.

SECTION - A

- Q.1 (A)** For the given network shown in figure 1, determine the current through $6\ \Omega$ and $5\ \Omega$ resistance using mesh analysis. [6]
CO1 BL5

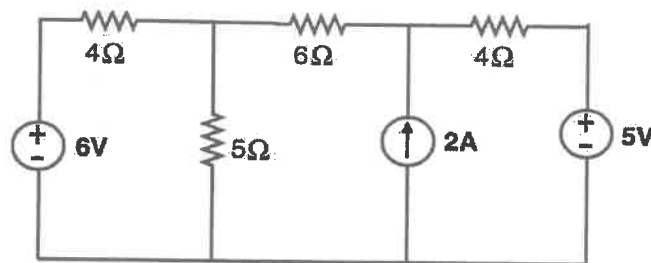


Fig. 1

- Q.1 (B)** Write the node voltage equations and determine currents in each branch for the network shown in Fig. 2. [6]
CO1 BL5

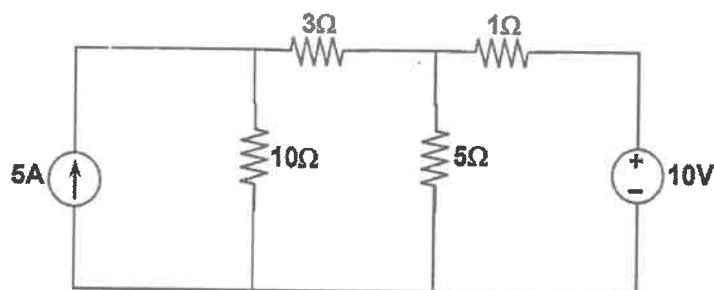


Fig. 2

- Q.1 (C)** Explain the concept of source transformation. [4]
CO1 BL2

- Q.2 (A)** Use star-delta transformation to determine the equivalent resistance between terminal pair A-B of the network shown in Fig. 3. [6]
CO1 BL5

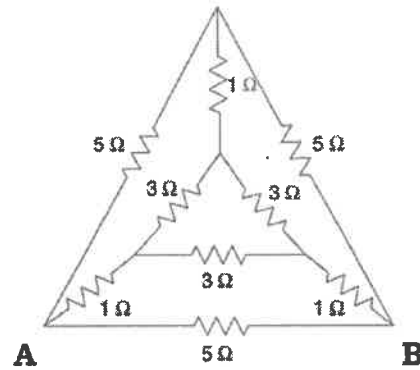


Fig. 3

- Q.2 (B)** Apply superposition theorem to estimate the current through 2Ω resistor in Fig. 4. [6]
CO1 BL5

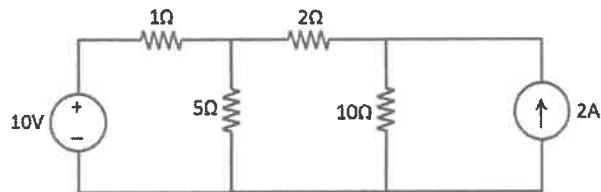


Fig.4

- Q.2 (C)** A $2\mu\text{F}$ capacitor is connected by closing a switch to a supply of 100V through a $100\text{ M}\Omega$ series resistance. Evaluate: (i) Time constant (ii) Initial charging current (iii) Initial rate of rise of voltage across capacitor (iv) Voltage across the capacitor 6 sec after the switch has been closed. [4]
CO1 BL5

- Q.3 (A)** Deduce the expression for the frequency at which voltage across inductor and the voltage across capacitor becomes maximum in a RLC series circuit excited by a sinusoidal source with variable frequency. Supplement the arguments with suitable phasor diagram. Write any two properties of RLC series resonant circuit. [6]
CO2 BL5

- Q.3 (B)** Estimate the RMS value, average value and form factor of the periodic waveform shown in Fig. 6. [6]
CO2 BL5

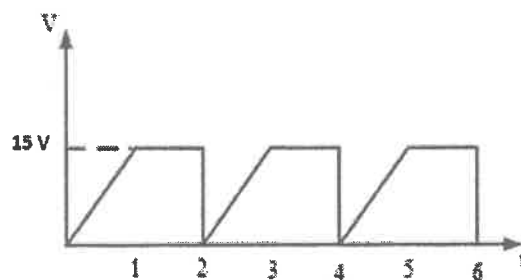


Fig. 6

- Q.3 (C)** A series RC circuit is excited by a sinusoidal source at a frequency of 'f' hertz. If the applied voltage is $e(t) = V_m \sin \omega t$. Derive the expression for current in trigonometric form. Support the mathematical expressions with suitable phasor diagram. Draw the impedance triangle, voltage triangle and power triangle. [6]
CO2 BL5

SECTION - B

- Q.4 (A)** If a three phase balanced delta connected load is supplied from a balanced three phase voltage source, derive the relationship between (i) line voltage and phase voltage (ii) line current and phase current. Draw the phasor diagram. [6]
CO2 BL5

- Q.4 (B)** Three similar coils each having a resistance of 4Ω and an inductance of $0.03H$ are connected in star to a $415 V$, 3-phase, $50Hz$ supply. Calculate the phase voltage, line voltage, phase current, line current, power factor and total power absorbed. [6]
CO2 BL5

- Q.4 (C)** A 3-phase induction motor load has a power factor of 0.4 lagging. Two wattmeters connected to measure power shows the input as $25 kW$. Estimate the reading of each wattmeter. [4]
CO2 BL5

- Q.5 (A)** Draw and explain the working of a full wave bridge rectifier with suitable waveforms. [6]
CO3 BL2

- Q.5 (B)** The positive shunt clipper shown in Fig. 7 below has the input waveform as indicated. Determine the value of V_{out} for each of the input alternations. [6]
CO3 BL5

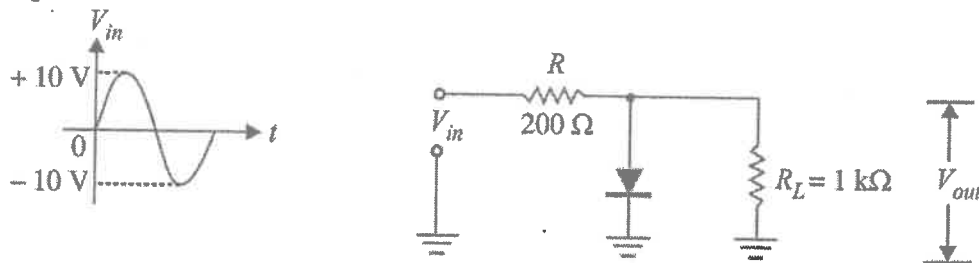


Fig. 7

- Q.5 (C)** Write comparison between analog circuit and digital circuits. [4]
CO3 BL2

- Q.6 (A)** Explain half adder circuit with neat sketch and its truth table. [6]
CO4 BL2

- Q.6 (B)** Solve the following boolean expressions and represent them using suitable logic circuit. [6]
CO4 BL3

i) $Y = A + \bar{A} \cdot B$

ii) $Y = A \cdot B + A \cdot \bar{B} + B \cdot C$

iii) $Y = A \cdot B + A \cdot B \cdot C + A \cdot B \cdot \bar{C}$

- Q.6 (C)** i) Convert $(1111011011)_2$ into its equivalent hexadecimal number. [6]
CO4 BL3
ii) Convert $(755)_8$ into its equivalent decimal number.
iii) Convert $(352)_{10}$ into its equivalent binary number.

Nirma University

Institute of Technology

Semester End Examination (IR/RPR), December - 2024
B. Tech. in All Programmes / Int. B. Tech. (CSE) - MBA, Semester-I/II
Bachelor of Science (CSE), Semester-I
1EE801CC22 / 1EE801 Electrical Science

Roll /
Exam No.

Supervisor's initial
with date

Time: 3 Hours

Max. Marks: 100

Instructions:

1. Attempt all questions.
2. Use section-wise separate answer book.
3. Figures to right indicate full marks.
4. Draw neat sketches wherever necessary.
5. Assume suitable additional data, if required.
6. All symbols and notations have their usual meaning.

SECTION - A

- Q.1 (A)** Apply nodal analysis to determine the current through $4\ \Omega$ resistor in the circuit shown in Fig.1 [6]
CO1 BL3

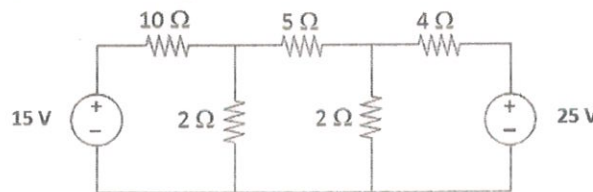


Fig. 1

- Q.1 (B)** Determine the power dissipation in $4\ \Omega$ resistor of the circuit shown in Fig. 2 using mesh analysis. [6]
CO1 BL5

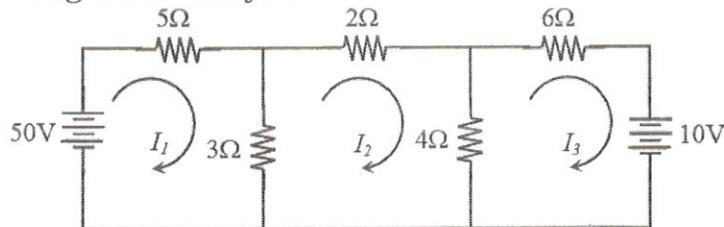


Fig. 2

- Q.1 (C)** A series R – C circuit is connected through a switch S to a dc supply of V volts. For such a circuit, deduce an expression for the variation of voltage across the capacitor plates when the capacitor is charging. [4]
CO1 BL5

- Q.2 (A)** Evaluate the current I in the circuit shown in Fig. 3 using star – delta transformation. [6]
CO1 BL5

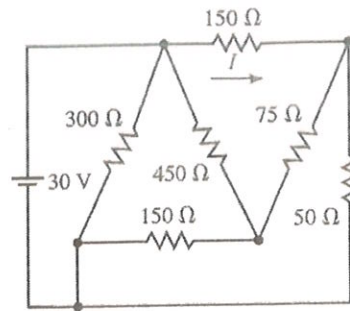


Fig. 3

- Q.2 (B)** Determine the current I_o using superposition theorem for the network shown in Fig. 4. [6]
CO1 BL5

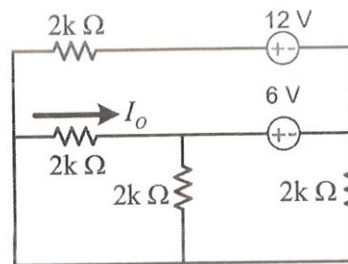


Fig. 4

- Q.2 (C)** A $2\mu\text{F}$ capacitor is charged to 600 V. If the capacitor is then discharged to 450V, estimate, how much energy has been left on the capacitor. [4]
CO1 BL5

- Q.3 (A)** Deduce the expression for equivalent inductance of two inductors connected in series for additive mutual coupling. [6]
CO2 BL5

- Q.3 (B)** Determine the form factor of the waveform shown in Fig. 5. [6]
CO2 BL5

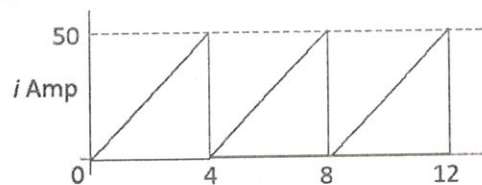


Fig. 5

- Q.3 (C)** Define the following terms with reference to a sinusoidal waveform: [6]
CO2 BL1
- i) Instantaneous Value
 - ii) Alteration
 - iii) Phase Difference
 - iv) Time Period
 - v) RMS value
 - vi) Frequency

SECTION - B

- Q.4 (A)** Estimate the resultant of the following voltages when they are added together. Draw the phasor diagram. [6]
CO2 BL5

$$V_1 = 4\sqrt{2} \sin(\omega t + 135^\circ)$$

$$V_2 = -4\sqrt{3} \sin(\omega t + 60^\circ)$$

$$V_3 = 4 \cos(\omega t - 150^\circ)$$

- Q.4 (B)** Three similar coils each having a resistance of 5Ω and an inductance of $0.02H$ are connected in delta to a $440V$, 3-phase, $50Hz$ supply. Calculate the phase voltage, line voltage, phase current, line current, power factor and total power absorbed. [6]
CO2 BL5

- Q.4 (C)** A 3-phase induction motor load has a p.f. of 0.397 lagging. Two wattmeters connected to measure power shows the input as $30 kW$. Find the reading of each wattmeter. [4]
CO2 BL5

- Q.5 (A)** Draw and explain the working of a center tap rectifier. Deduce its expression for efficiency. [6]
CO3 BL5

- Q.5 (B)** Discuss the working of diode as clipper and clamper. [6]
CO3 BL2

- Q.5 (C)** Design a full adder circuit and discuss its operation in detail. [4]
CO3 BL6

- Q.6 (A)** Evaluate the Boolean expression for the output Y for the logic circuit shown in Fig.6. Also write the truth table. [6]
CO4 BL5

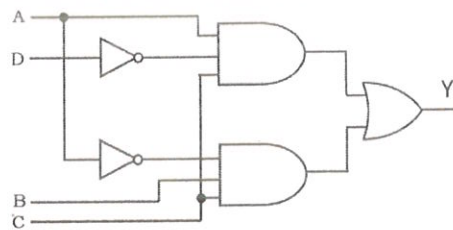


Fig. 6

- Q.6 (B)** Design X-OR gate using NAND gate only. [6]
CO4 BL6

Simplify the following Boolean expressions:

(i) $Y = \bar{A}\bar{B}C + A\bar{B}C + AB\bar{C} + ABC$ (ii) $Y = AB + A(B + C) + B(B + C)$

- Q.6 (C)** i) Convert octal number $(24.6)_8$ to the equivalent decimal number [6]
CO4 BL3
ii) Convert $(177)_{10}$ to its 8-bit binary equivalent by first converting to octal.
iii) Convert decimal number 378 to a 16-bit number by first converting to hexadecimal

Nirma University

Institute of Technology

Supplementary Examination (SPE), February - 2025

B. Tech. in All Programmes, Semester-I

Bachelor of Science (CSE), Semester-I

1EE801CC22: ELECTRICAL SCIENCE

Roll /
Exam No.

Supervisor's initial
with date

Time: 3 Hours

Max. Marks: 100

Instructions:

1. Attempt all questions.
2. Use section-wise separate answer book.
3. Figures to right indicate full marks.
4. Draw neat sketches wherever necessary.
5. Assume suitable additional data if required.
6. All symbols and notations have their usual meaning.

SECTION - A

- Q.1 (A)** Apply star delta transformation to find the equivalent resistance between the terminal pair X-Z for the circuit shown in Fig. 1. [6]
CO1 BL3

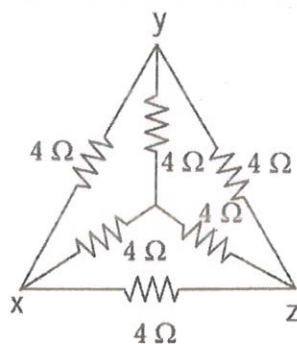


Fig. 1

- Q.1 (B)** Determine the current delivered by the source of 10 volts in the network shown in Fig. 2. [6]
CO1 BL5

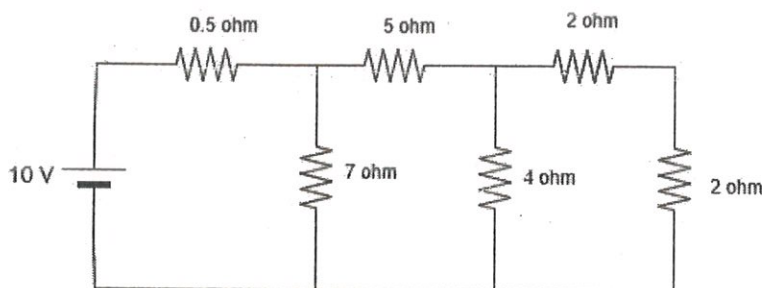


Fig. 2

- Q.1 (C)** A 10 μF capacitor is connected in series with 1 $\text{M}\Omega$ resistor across the supply of 100 volts. Calculate: (i) time constant (ii) initial charging current (iii) voltage across capacitor after time equal to time constant and (iv) final steady state current. [4]
CO1 BL5

Q.2 (A) Explain the concept of source conversion. [4]
CO2 BL2

Q.2 (B) Apply Thevenin's theorem to find the current through $5\ \Omega$ resistor for the circuit shown in Fig. 3. [6]
CO1 BL3

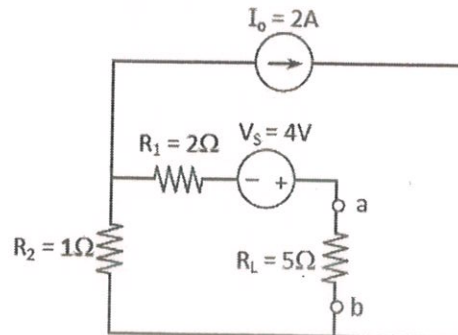


Fig. 3

Q.2 (C) Use nodal analysis to find the current through $5\ \Omega$ resistor in the network shown in Fig. 4. [6]
CO1 BL5

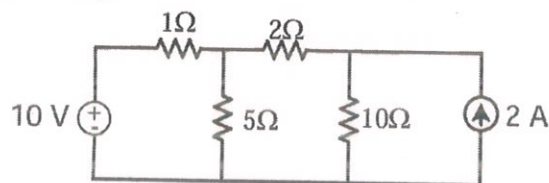


Fig. 4

Q.3 (A) Summarise the similarities between a magnetic circuit and electrical circuit. [6]
CO2 BL2

Q.3 (B) Explain with neat sketch the generation of sinusoidal voltage. [6]
CO2 BL2

Q.3 (C) Estimate the RMS value, average value, form factor and peak factor for the waveform shown in Fig. 5. [6]
CO2 BL5

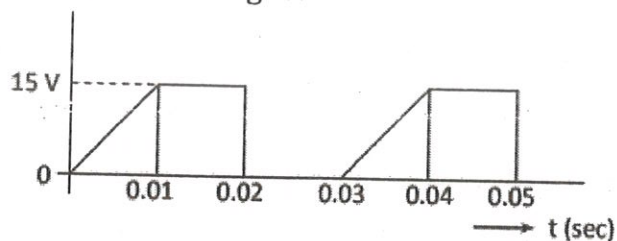


Fig. 5

SECTION - B

Q.4 (A) List few merits of three phase system over single-phase system. [4]
CO2 BL2

Q.4 (B) Define the following terms with reference to alternating current:
i) instantaneous value ii) maximum value iii) average value iv) time period. [4]
CO2 BL2

- Q.4 (C)** A 3-phase load consists of three star connected similar resistances, each of resistance of 50Ω . The supply is 400 V, 50 Hz. Calculate (i) line current (ii) total power consumed (iii) phase voltage (iv) power factor. [6]
CO2 BL5
- Q.5 (A)** Illustrate with neat sketch the working of half wave rectifier circuit and draw its input and output waveforms. [6]
CO3 BL2
- Q.5 (B)** Explain any two special purpose diodes and mention their application areas. [6]
CO3 BL2
- Q.5 (C)** Compare bipolar junction transistor in common base, common emitter and common collector mode configurations. [6]
CO3 BL2
- Q.6 (A)** Design X-OR gate using NAND gate only. [6]
CO4 BL3
Simplify the following Boolean expressions:
i) (i) $Y = \bar{A}\bar{B}C + A\bar{B}C + AB\bar{C} + ABC$ (ii) $Y = AB + A(B + C) + B(B + C)$
- Q.6 (B)** Give reasons, why digital circuits are preferred over analog circuits? [6]
CO4 BL2
- Q.6 (C)** Design a full adder using half adders. [6]
CO4 BL6

Nirma University

Institute of Technology

Supplementary Examination (SPE), July - 2025

B. Tech. in Ch / EC / CSE, Semester-I

B. Tech. in CL / ME / EE / CSE / AI&ML, Semester-II

1EE801CC22 Electrical Science

Roll /
Exam No.

Supervisor's initial
with date

Time: 3 Hours

Max. Marks: 100

Instructions:

1. Attempt all questions.
2. Use section-wise separate answer book.
3. Figures to right indicate full marks.
4. Draw neat sketches wherever necessary.
5. Assume suitable additional data, if required.
6. All symbols and notations have their usual meaning.

SECTION - A

- Q.1 (A)** Compute the potential difference across the $4\ \Omega$ resistor for the network shown in Fig. 1 using nodal analysis. [6]
CO1 BL5

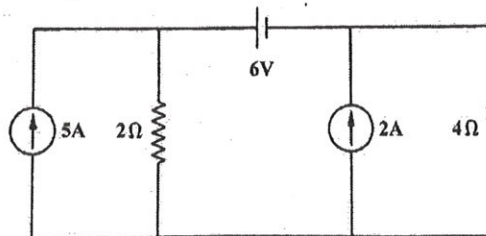


Fig. 1

- Q.1 (B)** Use source transformation and mesh analysis to determine the current through $3\ \Omega$ resistor for the network shown in Fig. 2. [6]
CO1 BL5

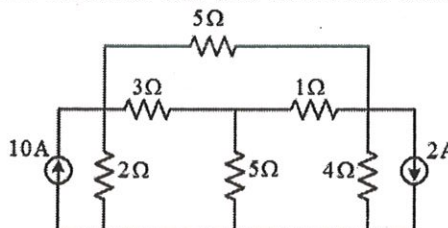


Fig. 2

- Q.1 (C)** State and explain superposition theorem. [4]
CO1 BL2

- Q.2 (A)** Apply star-delta transformation to find the current delivered by the source of 196 V for the circuit shown in Fig. 3. [6]
CO1 BL3

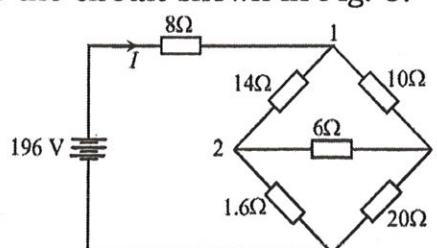


Fig. 3

Q.2 (B)
CO1 BL3

Apply Norton's theorem to find the current through $5\ \Omega$ resistor for the circuit shown in Fig. 4.

[6]

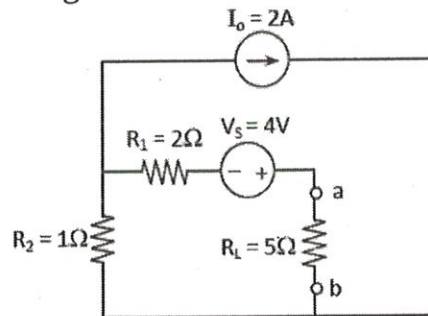


Fig. 4

Q.2 (C)
CO1 BL5

A $5\ \mu\text{F}$ capacitor is connected by closing a switch to a supply of 150 volts through a $80\ \text{M}\Omega$ series resistance. Evaluate: (i) Time constant (ii) Initial charging current (iii) Initial rate of rise of voltage across capacitor (iv) Voltage across the capacitor 6 sec after the switch has been closed.

[4]

Q.3 (A)
CO2 BL5

For the AC network shown in Fig. 5, calculate:

[6]

- Supply current, and
- Real power consumed.

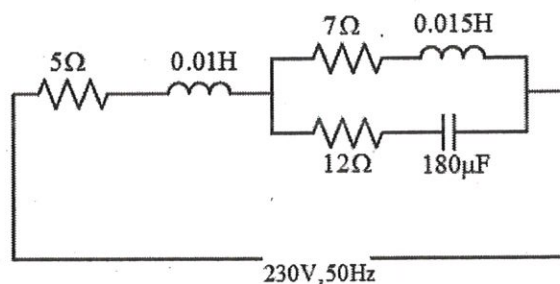


Fig. 5

Q.3 (B)
CO2 BL3

Make use of complex algebra to find the following in polar form :

[6]

- Add $(40 + j20)$ to $(20 + j120)$
- Subtract $(10 + j30)$ from $(20 - j20)$
- Multiply $(15 + j20)$ with $(20 + j30)$
- Divide $(6 + j7)$ by $(5 + j3)$

Q.3 (C)
CO2 BL5

An alternating current is given by: $i(t) = 10 \sin 942t$ Amperes
Determine:

[6]

- the frequency,
- time period,
- time taken from $t = 0$ for the current to reach a value of 6 A for the first time.

SECTION - B

- Q.4 (A)** If a three phase balanced star connected load is supplied from a balanced three phase voltage source, derive the relationship between (i) line voltage and phase voltage (ii) line current and phase current. Draw the phasor diagram. [6]
CO2 BL5
- Q.4 (B)** Three similar coils each having a resistance of $3\ \Omega$ and an inductance of $0.04\ \text{H}$ are connected in star to a $415\ \text{V}$, 3-phase, $50\ \text{Hz}$ supply. Calculate the phase voltage, line voltage, phase current, line current, power factor and total power absorbed. [6]
CO2 BL5
- Q.4 (C)** A 3-phase induction motor load has a pf of 0.45 lagging. Two wattmeters connected to measure power shows the input as $35\ \text{kW}$. Estimate the reading of each wattmeter. [4]
CO2 BL5
- Q.5 (A)** Draw and explain the working of a half wave rectifier with suitable waveforms. [6]
CO3 BL2
- Q.5 (B)** Explain positive biased clipper and negative biased clipper with neat sketches. [6]
CO3 BL2
- Q.5 (C)** Write short notes on the following: [4]
CO3 BL2
(a) Zener diode (b) Photo diode
- Q.6 (A)** Write the Boolean expression for the output Y for the logic circuit shown in Fig.6. Also write the truth table. [6]
CO4 BL3

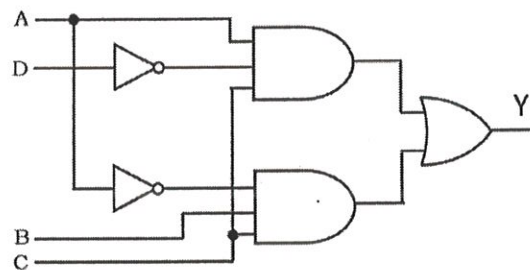


Fig. 6

- Q.6 (B)** Explain full adder circuit with neat and clean diagram and truth table. [6]
CO4 BL3
- Q.6 (C)** Solve the following Boolean expressions: [6]
CO4 BL3
i) $Y = \bar{A}\bar{B}C + A\bar{B}C + AB\bar{C} + ABC$
ii) $Y = AB + A(B + C) + B(B + C)$
iii) $Y = AC\bar{D} + \bar{A}B(CD + BC)$

Nirma University

Institute of Technology

Semester End Examination (IR/RPR), April - 2025

B. Tech. in All Programmes, Semester - I / II

Int. B. Tech. (CSE) - MBA, Semester - I / II

Bachelor of Science (CSE), Semester - I

1EE801CC22 / 1EE801 Electrical Science

Roll /
Exam No.

Supervisor's initial
with date

Time: 3 Hours

Max. Marks: 100

Instructions:

1. Attempt all questions.
2. Use section-wise separate answer book.
3. Figures to right indicate full marks.
4. Draw neat sketches wherever necessary.
5. Assume suitable additional data, if required.
6. All symbols and notations have their usual meaning.

SECTION - A

- Q.1 (A)** For the given network shown in figure 1, determine the current through $6\ \Omega$ and $5\ \Omega$ resistance using mesh analysis. [6]
CO1 BL5

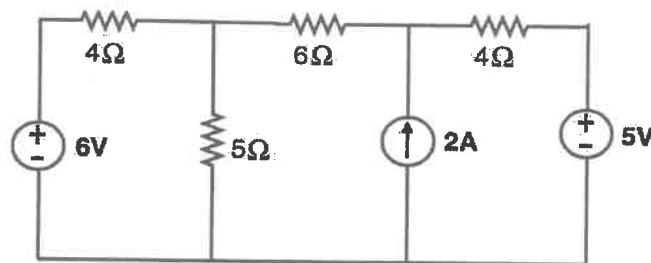


Fig. 1

- Q.1 (B)** Write the node voltage equations and determine currents in each branch for the network shown in Fig. 2. [6]
CO1 BL5

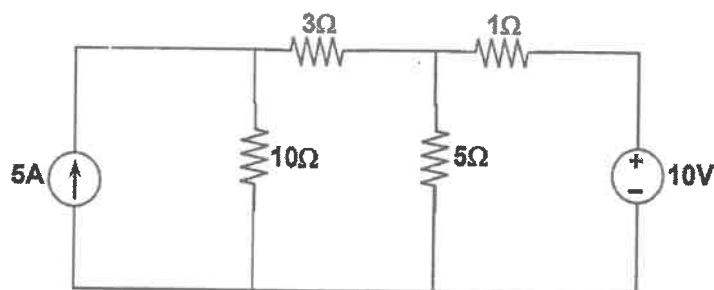


Fig. 2

- Q.1 (C)** Explain the concept of source transformation. [4]
CO1 BL2

- Q.2 (A)** Use star-delta transformation to determine the equivalent resistance between terminal pair A-B of the network shown in Fig. 3. [6]
CO1 BL5

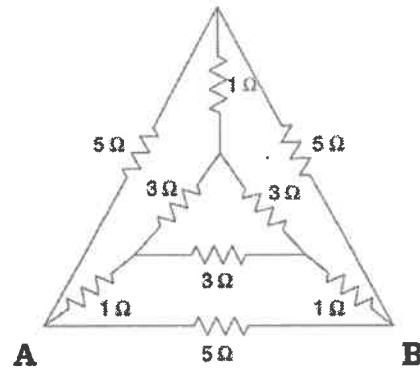


Fig. 3

- Q.2 (B)** Apply superposition theorem to estimate the current through 2Ω resistor in Fig. 4. [6]
CO1 BL5

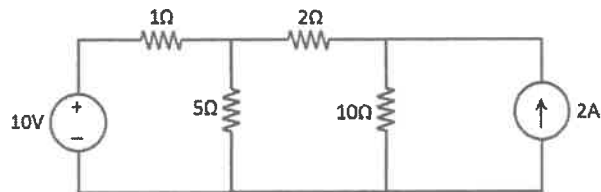


Fig.4

- Q.2 (C)** A $2\mu\text{F}$ capacitor is connected by closing a switch to a supply of 100V through a $100\text{ M}\Omega$ series resistance. Evaluate: (i) Time constant (ii) Initial charging current (iii) Initial rate of rise of voltage across capacitor (iv) Voltage across the capacitor 6 sec after the switch has been closed. [4]
CO1 BL5

- Q.3 (A)** Deduce the expression for the frequency at which voltage across inductor and the voltage across capacitor becomes maximum in a RLC series circuit excited by a sinusoidal source with variable frequency. Supplement the arguments with suitable phasor diagram. Write any two properties of RLC series resonant circuit. [6]
CO2 BL5

- Q.3 (B)** Estimate the RMS value, average value and form factor of the periodic waveform shown in Fig. 6. [6]
CO2 BL5

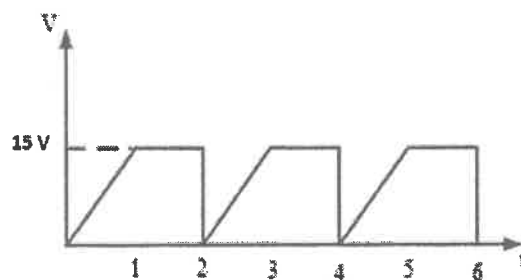


Fig. 6

- Q.3 (C)** A series RC circuit is excited by a sinusoidal source at a frequency of 'f' hertz. If the applied voltage is $e(t) = V_m \sin \omega t$. Derive the expression for current in trigonometric form. Support the mathematical expressions with suitable phasor diagram. Draw the impedance triangle, voltage triangle and power triangle. [6]
CO2 BL5

SECTION - B

- Q.4 (A)** If a three phase balanced delta connected load is supplied from a balanced three phase voltage source, derive the relationship between (i) line voltage and phase voltage (ii) line current and phase current. Draw the phasor diagram. [6]
CO2 BL5
- Q.4 (B)** Three similar coils each having a resistance of 4Ω and an inductance of 0.03H are connected in star to a 415 V , 3-phase, 50Hz supply. Calculate the phase voltage, line voltage, phase current, line current, power factor and total power absorbed. [6]
CO2 BL5
- Q.4 (C)** A 3-phase induction motor load has a power factor of 0.4 lagging. Two wattmeters connected to measure power shows the input as 25 kW . Estimate the reading of each wattmeter. [4]
CO2 BL5

- Q.5 (A)** Draw and explain the working of a full wave bridge rectifier with suitable waveforms. [6]
CO3 BL2
- Q.5 (B)** The positive shunt clipper shown in Fig. 7 below has the input waveform as indicated. Determine the value of V_{out} for each of the input alternations. [6]
CO3 BL5

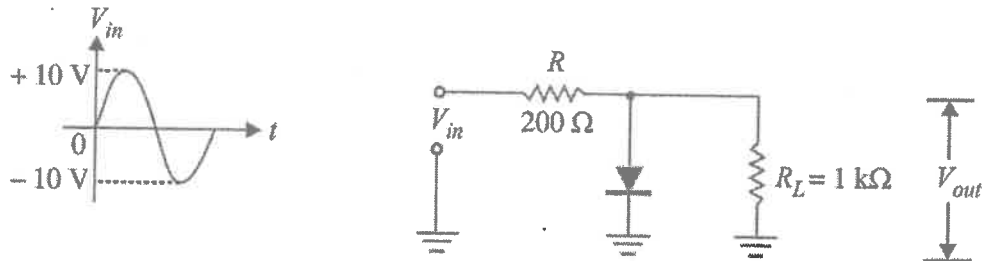


Fig. 7

- Q.5 (C)** Write comparison between analog circuit and digital circuits. [4]
CO3 BL2
- Q.6 (A)** Explain half adder circuit with neat sketch and its truth table. [6]
CO4 BL2
- Q.6 (B)** Solve the following boolean expressions and represent them using suitable logic circuit. [6]
CO4 BL3
- $Y = A + \bar{A} \cdot B$
 - $Y = A \cdot B + A \cdot \bar{B} + B \cdot C$
 - $Y = A \cdot B + A \cdot B \cdot C + A \cdot B \cdot \bar{C}$
- Q.6 (C)**
- Convert $(1111011011)_2$ into its equivalent hexadecimal number. [6]
 - Convert $(755)_8$ into its equivalent decimal number.
 - Convert $(352)_{10}$ into its equivalent binary number.

Nirma University

Institute of Technology

Semester End Examination (IR/RPR), December - 2024
B. Tech. in All Programmes / Int. B. Tech. (CSE) - MBA, Semester-I/II
Bachelor of Science (CSE), Semester-I
1EE801CC22 / 1EE801 Electrical Science

Roll /
Exam No.

Supervisor's initial
with date

Time: 3 Hours

Max. Marks: 100

Instructions:

1. Attempt all questions.
2. Use section-wise separate answer book.
3. Figures to right indicate full marks.
4. Draw neat sketches wherever necessary.
5. Assume suitable additional data, if required.
6. All symbols and notations have their usual meaning.

SECTION - A

- Q.1 (A)** Apply nodal analysis to determine the current through $4\ \Omega$ resistor in the circuit shown in Fig.1 [6]
CO1 BL3

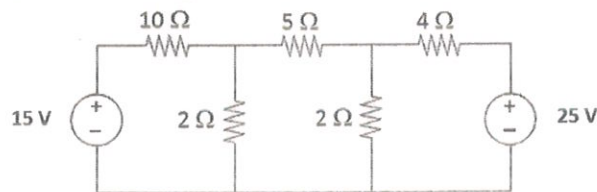


Fig. 1

- Q.1 (B)** Determine the power dissipation in $4\ \Omega$ resistor of the circuit shown in Fig. 2 using mesh analysis. [6]
CO1 BL5

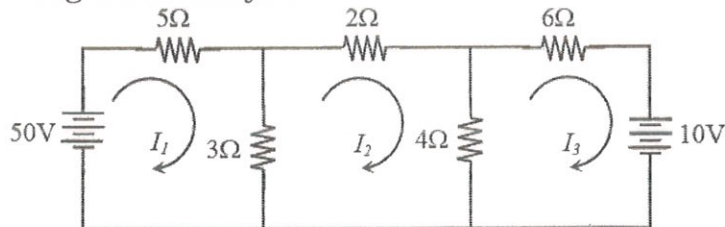


Fig. 2

- Q.1 (C)** A series R – C circuit is connected through a switch S to a dc supply of V volts. For such a circuit, deduce an expression for the variation of voltage across the capacitor plates when the capacitor is charging. [4]
CO1 BL5

- Q.2 (A)** Evaluate the current I in the circuit shown in Fig. 3 using star – delta transformation. [6]
CO1 BL5

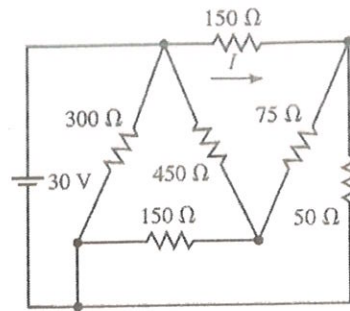


Fig. 3

- Q.2 (B)** Determine the current I_o using superposition theorem for the network shown in Fig. 4. [6]
CO1 BL5

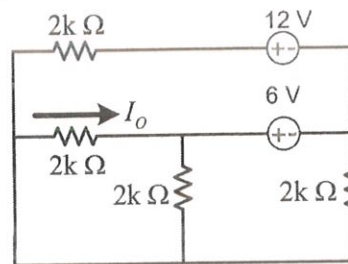


Fig. 4

- Q.2 (C)** A $2\mu\text{F}$ capacitor is charged to 600 V. If the capacitor is then discharged to 450V, estimate, how much energy has been left on the capacitor. [4]
CO1 BL5

- Q.3 (A)** Deduce the expression for equivalent inductance of two inductors connected in series for additive mutual coupling. [6]
CO2 BL5

- Q.3 (B)** Determine the form factor of the waveform shown in Fig. 5. [6]
CO2 BL5

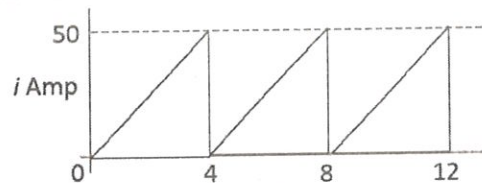


Fig. 5

- Q.3 (C)** Define the following terms with reference to a sinusoidal waveform: [6]
CO2 BL1
- i) Instantaneous Value
 - ii) Alteration
 - iii) Phase Difference
 - iv) Time Period
 - v) RMS value
 - vi) Frequency

SECTION - B

- Q.4 (A)** Estimate the resultant of the following voltages when they are added together. Draw the phasor diagram. [6]
CO2 BL5

$$V_1 = 4\sqrt{2} \sin(\omega t + 135^\circ)$$

$$V_2 = -4\sqrt{3} \sin(\omega t + 60^\circ)$$

$$V_3 = 4 \cos(\omega t - 150^\circ)$$

- Q.4 (B)** Three similar coils each having a resistance of 5Ω and an inductance of $0.02H$ are connected in delta to a $440V$, 3-phase, $50Hz$ supply. Calculate the phase voltage, line voltage, phase current, line current, power factor and total power absorbed. [6]
CO2 BL5

- Q.4 (C)** A 3-phase induction motor load has a p.f. of 0.397 lagging. Two wattmeters connected to measure power shows the input as $30 kW$. Find the reading of each wattmeter. [4]
CO2 BL5

- Q.5 (A)** Draw and explain the working of a center tap rectifier. Deduce its expression for efficiency. [6]
CO3 BL5

- Q.5 (B)** Discuss the working of diode as clipper and clamper. [6]
CO3 BL2

- Q.5 (C)** Design a full adder circuit and discuss its operation in detail. [4]
CO3 BL6

- Q.6 (A)** Evaluate the Boolean expression for the output Y for the logic circuit shown in Fig.6. Also write the truth table. [6]
CO4 BL5

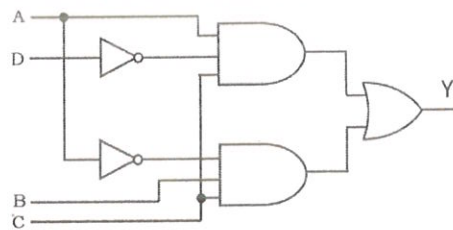


Fig. 6

- Q.6 (B)** Design X-OR gate using NAND gate only. [6]
CO4 BL6

Simplify the following Boolean expressions:

(i) $Y = \bar{A}\bar{B}C + A\bar{B}C + AB\bar{C} + ABC$ (ii) $Y = AB + A(B + C) + B(B + C)$

- Q.6 (C)** [6]
CO4 BL3
- Convert octal number $(24.6)_8$ to the equivalent decimal number
 - Convert $(177)_{10}$ to its 8-bit binary equivalent by first converting to octal.
 - Convert decimal number 378 to a 16-bit number by first converting to hexadecimal

Nirma University

Institute of Technology

Semester End Examination (IR/RPR), December - 2023

B. Tech. in All Programmes, Semester-I/II

Int. B. Tech. (CSE) – MBA, Semester-I

Bachelor of Science (Computer Science and Engineering), Semester-I

1EE801 Electrical Science

Roll /
Exam No.

Supervisor's initial
with date

Time: 3 Hours

Max. Marks: 100

Instructions:

1. Attempt all questions.
2. Use section-wise separate answer book.
3. Figures to right indicate full marks.
4. Draw neat sketches wherever necessary.
5. Assume suitable additional data if required.
6. All symbols and notations have their usual meaning.

SECTION - A

- Q.1 (A)** Apply star delta transformation to find the equivalent resistance between the terminal pair a-b for the circuit shown in Fig. 1. [6]
CO1 BL5

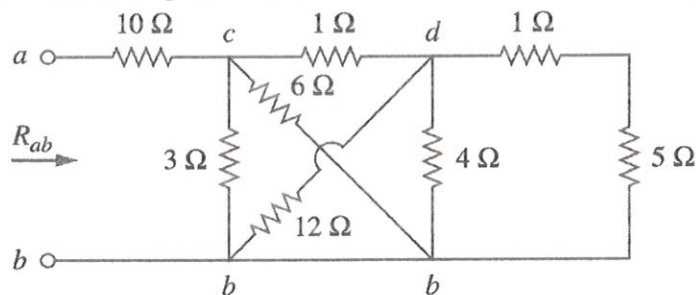


Fig. 1

- Q.1 (B)** For the circuit shown in Fig. 2, find: (a) v_1 and v_2 (b) power dissipated in $3\text{ k}\Omega$ and $20\text{ k}\Omega$ resistors, and (c) power supplied by the current source. [6]
CO1 BL5

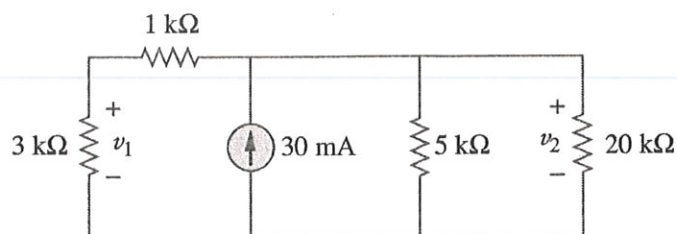


Fig. 2

- Q.1 (C)** Three capacitors of $1\text{ }\mu\text{F}$, $2\text{ }\mu\text{F}$ and $3\text{ }\mu\text{F}$ are connected in series across a supply of 100 V . Find the equivalent capacitance of the combination and energy stored in each capacitor. [4]
CO1 BL5
- Q.2 (A)** State and explain Superposition theorem using illustrative example. [6]
CO1 BL2

- Q.2 (B)** Use mesh analysis to find the current delivered by 240 V source for the network shown in Fig. 3. [6]
CO1 BL3

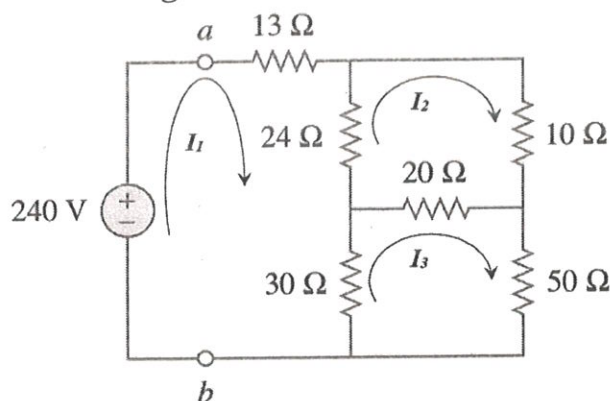


Fig. 3

- Q.2 (C)** A capacitor 'C' in series with a resistor 'R' and the series combination is connected to a DC source of 'E' volts. Find an expression for the charge 'Q' as a function of time. [4]
CO1 BL3

- Q.3 (A)** Define the following terms with respect to magnetic circuit. [6]
CO2 BL2 (i) MMF, (ii) Permeance, (iii) Reluctance, (iv) Fringing.

- Q.3 (B)** A large coil of inductance 1.405 H and resistance 40 Ω is connected in series with a capacitor of 20 μF. Calculate the frequency at which the circuit resonates. If a voltage of 100 V at the corresponding frequency is applied to the circuit, calculate the current drawn from the supply and voltage across the coil and across the capacitor. [6]
CO2 BL5

- Q.3 (C)** A circuit shown in Fig. 4 consists of the following in parallel: (i) A resistance of 500 Ω, (ii) an inductance of 2 H, (iii) A capacitance of 10 μF. A source of 200 V, 50 Hz is applied. Determine the current drawn from the source, active power, reactive power and the apparent power. [6]
CO2 BL5

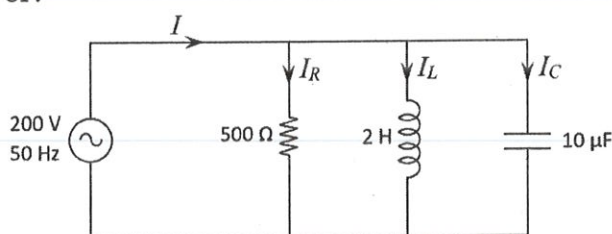


Fig. 4

SECTION - B

- Q.4 (A)** A three-phase balanced load connected across a three phase 400 V AC supply draws a line current 10 A. Two wattmeters are used to measure the input power. The ratio of two wattmeter readings is 2:1. Find the readings of the two wattmeters. [6]
CO2 BL5

Q.4 (B) Calculate the RMS value, average value and form factor of the function shown in Fig. 5. [6]
CO2 BL5

If $y = 10(1 - e^{-100t})$ for $0 < t < 0.1$ and;
 $y = 10e^{-50(t-0.1)}$ for $0.1 < t < 0.2$.

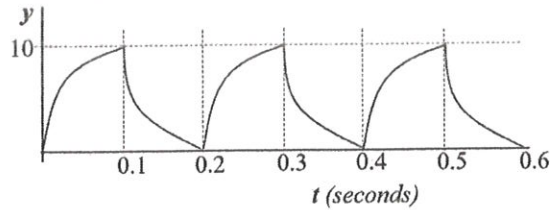


Fig. 5

Q.4 (C) Differentiate between balanced and unbalanced three phase loads. Give reasons why is an unbalanced load not normally used on 3 - phase 3-wire system? [4]
CO2 BL2

Q.5 (A) Draw the circuit for a common-emitter bipolar transistor amplifier and explain its working. [6]
CO3 BL2

Q.5 (B) Explain with neat sketches, the working of: [6]
CO3 BL2
(i) Half-wave rectifier, (ii) Centre-tap full-wave rectifier, (iii) Bridge type full-wave rectifier.

Q.5 (C) Write the comparison between astable multivibrator, bistable multivibrator and monostable multivibrator. [4]
CO3 BL2

Q.6 (A) i) Determine the decimal value of the binary number 10011010. [6]
CO4 BL3
ii) Add 45_{10} with 25_{10} using binary numbers.
iii) Determine the MSB and the LSB of 50_{10} when expressed as an Octal number.

Q.6 (B) Draw a logic circuit, incorporating any gates of your choice, which will produce an output 1 when its two inputs are different. Also draw a logic circuit, incorporating only NOR gates, which will perform the same function. [6]
CO4 BL2

Q.6 (C) For the given logic circuit of Fig. 6, obtain the simplified output expression. Write the truth table for the same. [6]
CO4 BL3

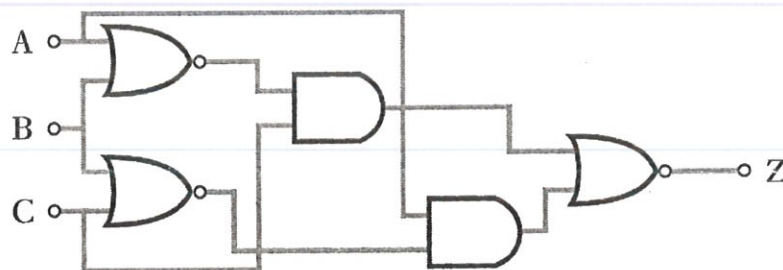


Fig. 6

Nirma University

Institute of Technology

Semester End Examination (IR/RPR), June - 2023

B. Tech. in CL / CH / ME / EE, Semester-II

B. Tech. in EI / EC / CSE, Semester-I

Int. B. Tech. (CSE) - MBA, Semester-II

1EE801 Electrical Science

Roll /

Exam No.

Supervisor's initial
with date

Time: 3 Hours

Max. Marks: 100

Instructions:

1. Attempt all questions.
2. Use section-wise separate answer book.
3. Figures to right indicate full marks.
4. Draw neat sketches wherever necessary.
5. Assume suitable additional data if required.
6. All symbols and notations have their usual meaning.

SECTION - A

- Q.1 (A)** Use mesh analysis to find the current through each resistor in the network shown in Fig. 1. [6]
CO1 BL4

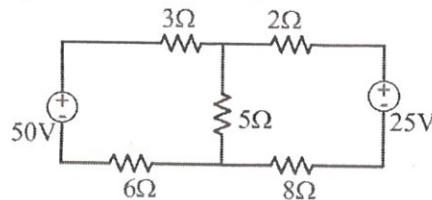


Fig. 1

- (B)** Use suitable method to find the current through 10 Ω resistor in the network shown in Fig. 2. [6]
CO1 BL4

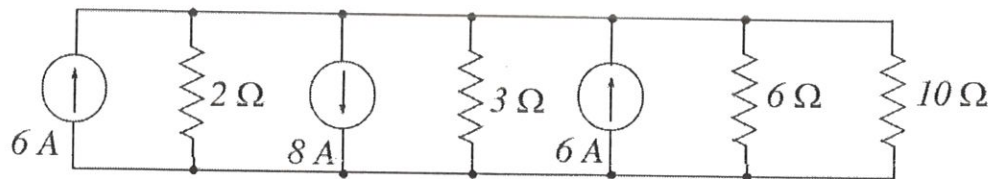


Fig. 2

- (C)** Draw a neat sketch of RC series circuit excited by a DC source. Write the equations for charging and discharging of capacitor. Draw the nature of graph showing voltage across resistor and voltage across capacitor. [4]
CO1 BL2
- Q.2 (A)** Derive an expression for the equivalent inductance when two inductances are connected in parallel opposition. [4]
CO2 BL5

- (B) Use star delta transformation to find the resistance between terminal pair P-Q of the network shown in Fig. 3. [6]
CO1 BL4

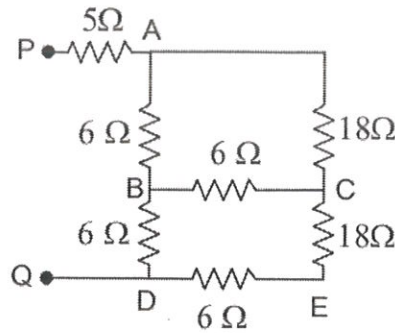


Fig. 3

- (C) Use Superposition theorem to find the current through 1 Ω resistor for the network shown in Fig. 4. [6]
CO1 BL4

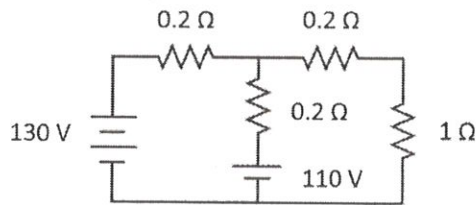


Fig. 4

- Q.3 (A)** Explain the concept of composite series and composite parallel magnetic circuit. How will you find the mean length and reluctances of various sections composed of different magnetic material? What is the effect of air gap in magnetic circuits? Illustrate with neat sketch. [6]
CO2 BL2
- (B) An iron ring of 300 cm mean circumference with a cross section of 5 cm² is wound uniformly with 350 turns of wire. Estimate the current required to produce a flux of 0.5 milli-Wb in iron. Assume relative permeability of iron as 400. [6]
CO2 BL5
- (C) Evaluate the average and RMS value for the periodic wave shown in Fig. 5 [6]
CO2 BL5

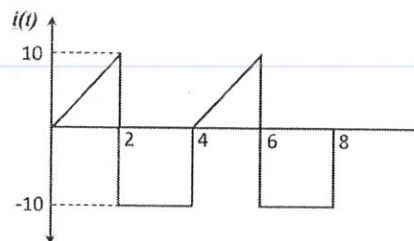


Fig. 5

SECTION - B

- Q.4 (A)** Solve the following expressions and obtain the results in polar form. [4]
CO2 BL3
- $(12 + j 15) \times (18 - j 12)$
 - $(3 + j 4) \div (10 - j 8)$
 - $(5 + j 12) + (10 - j 12)$
 - $(100 + j 150) - (90 - j 85)$

(B)
CO2 BL2 What are the merits of three-phase system over single-phase system? [4]

(C)
CO2 BL5 The power drawn by 440 volts, 50 Hz, three phase induction motor on full load is measured by two-watt-meters which indicate 250 W and 1000 W respectively. Evaluate (i) the input power (ii) power factor (iii) current (iv) motor output if the efficiency is 80% (v) reactive power (vi) apparent power. [6]

Q.5 (A)
CO3 BL2 Explain the following terms with reference to a crystal diode.
(i) Forward current (ii) Reverse current (iii) peak inverse voltage [6]

(B)
CO3 BL2 Write short notes on (i) LED (ii) photo-diode (iii) Zener diode [6]

(C)
CO3 BL5 Figure 6 has the input waveform as indicated. Determine the value of V_{out} for each of the input alternations. [6]

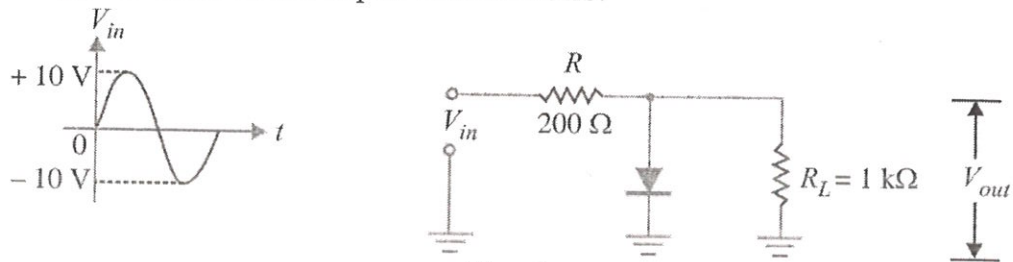


Fig. 6

Q.6 (A)
CO4 BL3 i) Convert the octal number $(24.6)_8$ to its equivalent decimal number. [6]
ii) Convert the hexa-decimal number $(9F2)_{16}$ to its equivalent binary number.
iii) Convert binary $(1101)_2$ to its equivalent decimal number.

(B)
CO4 BL5 Determine the complement of the following Boolean expressions:
i) $Y = \overline{A}\overline{B}C + A\overline{B}C + ABC\overline{C} + ABC$ (ii) $Y = AB + A(B + C) + B(B + C)$ [6]

(C)
CO4 BL4 Write the Boolean expression for the output Y for the logic circuit shown in Fig.7. Write the truth table. [6]

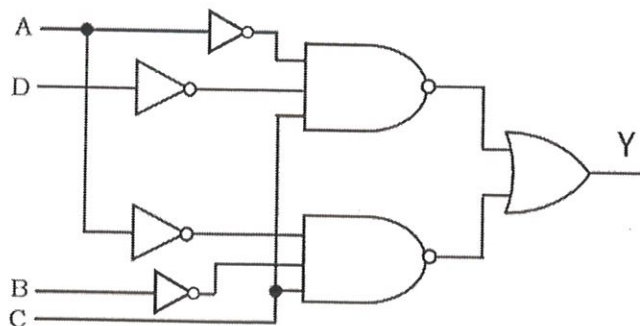


Fig. 7
